Ax no 7 Date > 31 st March 2021 Add Mahajan 19BE E0032

Aim > PCB design of crystal tester circuit
Apparatus required >

Name	Quantity	Library
Resistance	4 9	Designspark
Battery	1	Designspork
Ground	2	Designspork
Capacitance	4	Designspark
Diode	2	Designsfork
LED	1	Designspork
XTAL	1	Designspork
NFET	2	Resignspark

Description -> We used NFET as transister was causing issues resulting in test Soils.

Lohemater design -> Result -> Both the design and schematic diagram have been made and verified.











