
Hade Nah, King no 8 Date -> 7th April 2021 Aim - PCB Design of fire alarm circuit. Apparatus required -> Library Quantity Name Resistance Designsfork Battery Designsfirk La facitor Lesignsfork Ground Designsfork NMOS Lesignsfork We weren't able to use Description > Variable resistance and timers News of errors

kehematie diagram -

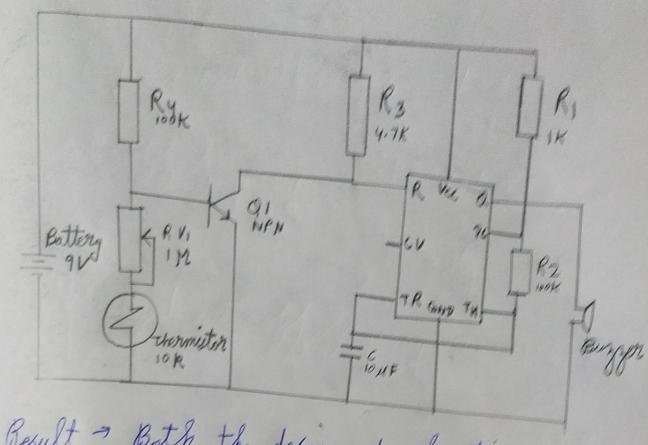

Result - Both the design and schematic digram have been made and verified.

